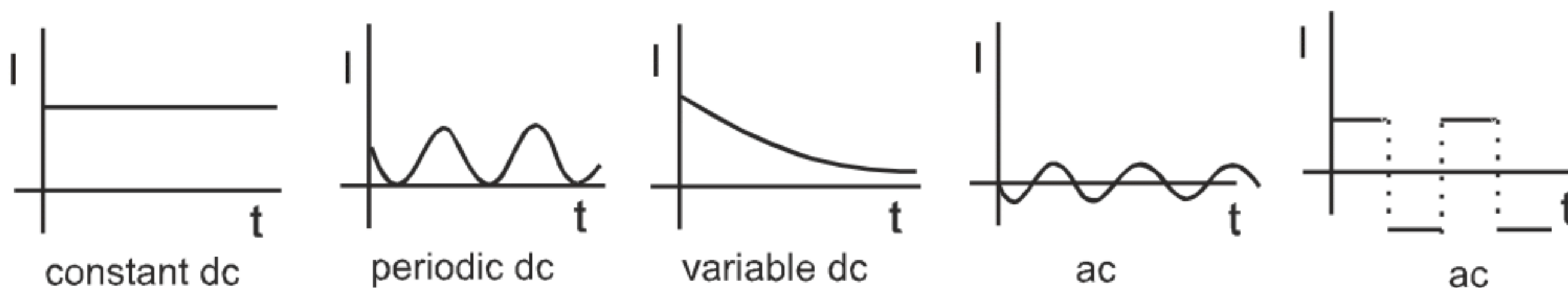


## 1. AC AND DC CURRENT :

A current that changes its direction periodically is called alternating current (AC). If a current maintains its direction constant it is called direct current (DC).




## 3. ROOT MEAN SQUARE VALUE:

Root Mean Square Value of a function, from  $t_1$  to  $t_2$ , is defined as

$$f_{\text{rms}} = \sqrt{\frac{\int_{t_1}^{t_2} f^2 dt}{t_2 - t_1}}.$$
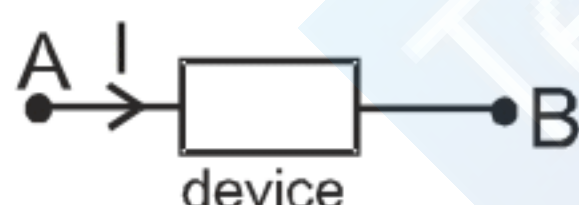
## 4. POWER CONSUMED OR SUPPLIED IN AN AC CIRCUIT:

$$\text{Average power consumed in a cycle} = \frac{\int_0^{2\pi} P dt}{2\pi} = \frac{1}{2} V_m I_m \cos \phi$$



$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos \phi = V_{\text{rms}} I_{\text{rms}} \cos \phi.$$

Here  $\cos \phi$  is called **power factor**.

## 5. SOME DEFINITIONS:

The factor  $\cos \phi$  is called **Power factor**.

$I_m \sin \phi$  is called **wattless current**.

**Impedance**  $Z$  is defined as  $Z = \frac{V_m}{I_m} = \frac{V_{\text{rms}}}{I_{\text{rms}}}$

$\omega L$  is called **inductive reactance** and is denoted by  $X_L$ .

$\frac{1}{\omega C}$  is called **capacitive reactance** and is denoted by  $X_C$ .


## 6. PURELY RESISTIVE CIRCUIT:

$$I = \frac{V_s}{R} = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t$$

$$I_m = \frac{V_m}{R}$$

$$I_{rms} = \frac{V_{rms}}{R}$$
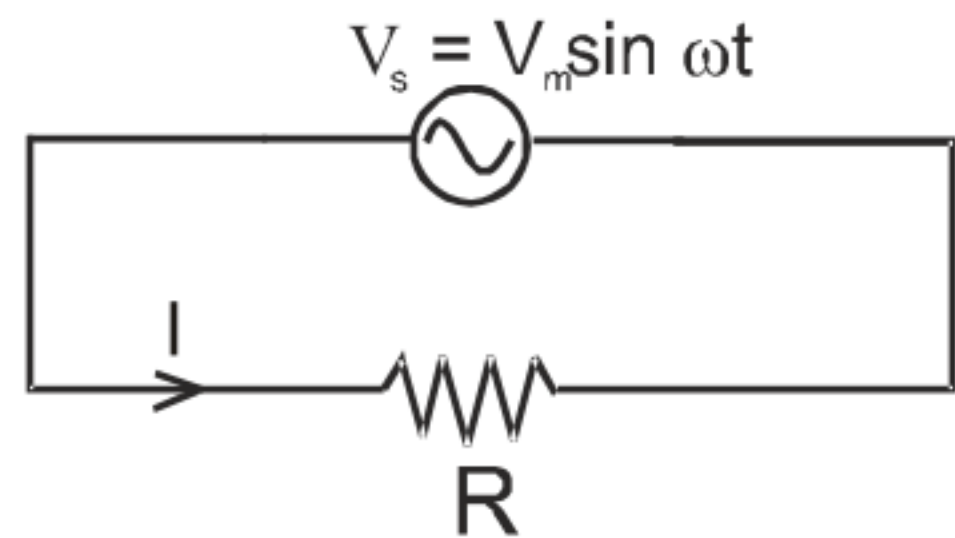
$$\langle P \rangle = V_{rms} I_{rms} \cos \phi = \frac{V_{rms}^2}{R}$$





## 7. PURELY CAPACITIVE CIRCUIT:


$$I = \frac{V_m}{1/\omega C} \cos \omega t$$

$$= \frac{V_m}{X_C} \cos \omega t = I_m \cos \omega t.$$
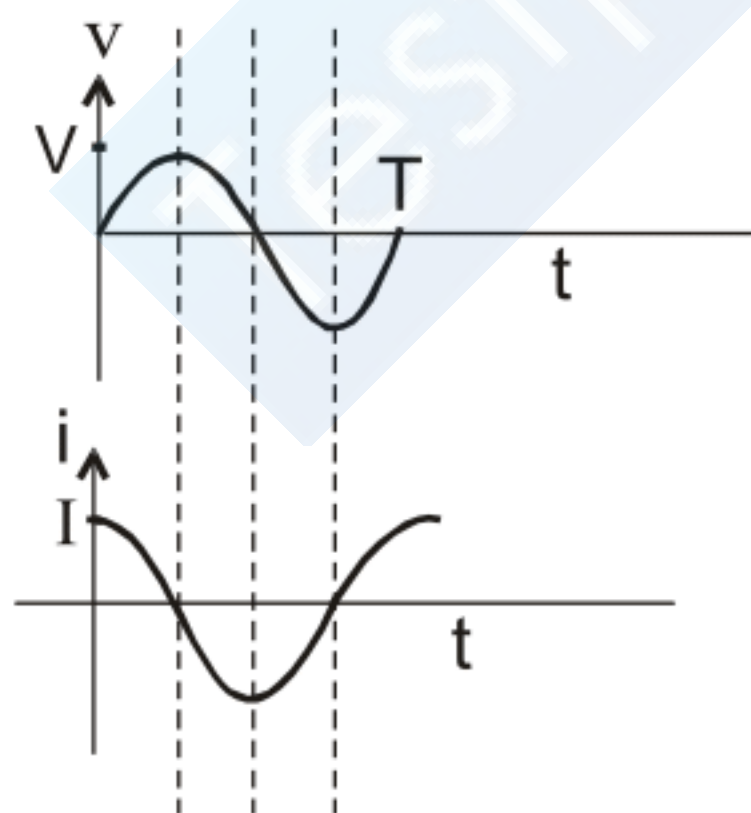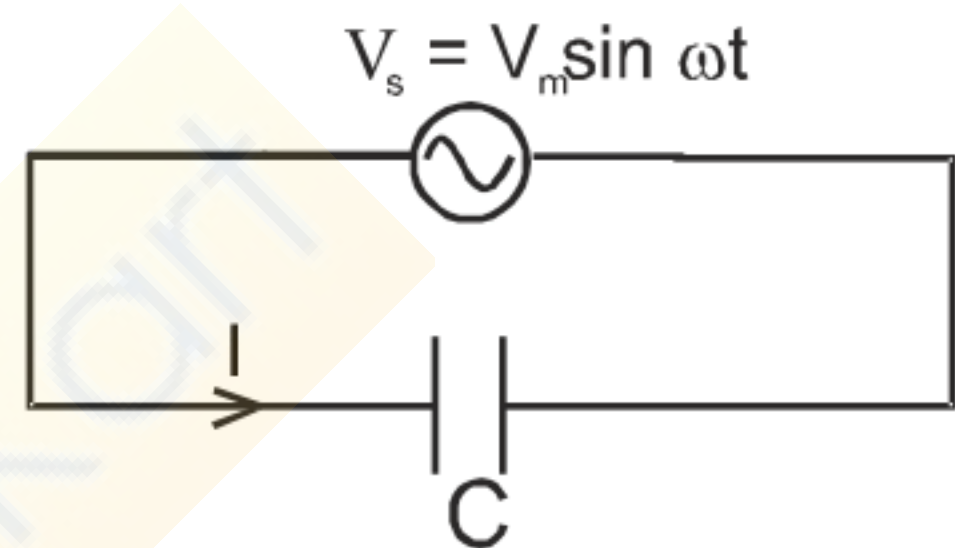
$$X_C = \frac{1}{\omega C} \text{ and is called capacitive reactance.}$$



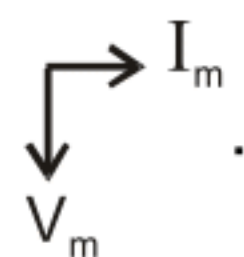$I_C$  leads by  $V_C$  by  $\pi/2$  Diagrammatically (phasor diagram) it is represented as



$$\text{Since } \phi = 90^\circ, \langle P \rangle = V_{rms} I_{rms} \cos \phi = 0$$