## Grouping of Capacitors.

Series grouping	Parallel grouping
(1) Charge on each capacitor remains same and equals to the main charge supplied by the battery $V = V_1 + V_2 + V_3$	(1) Potential difference across each capacitor remains same and equal to the applied $a_1$ potential difference $Q = Q_1 + Q_2 + Q_3$
(2) Equivalent capacitance	
$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \text{ or } C_{eq} = (C_1^{-1} + C_2^{-1} + C_3^{-1})^{-1}$	(2) $C_{eq} = C_1 + C_2 + C_3$
(3) In series combination potential difference and energy distribution in the reverse ratio of capacitance i.e., $V \propto \frac{1}{C}$ and $U \propto \frac{1}{C}$ .	(3) In parallel combination charge and energy distributes in the ratio of capacitance i.e. Q $\propto$ C and U $\propto$ C
(4) If two capacitors having capacitances $C_1$ and $C_2$ are connected in series then $C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{\text{Multiplication}}{\text{Addition}}$ $V_1 = \left(\frac{C_1}{C_1 + C_2}\right) V \text{ and } V_2 = \left(\frac{C_2}{C_1 + C_2}\right) V$	(4) If two capacitors having capacitance C <sub>1</sub> and C <sub>2</sub> respectively are connected in parallel then $C_{eq} = C_1 + C_2$ $Q_1 = \left(\frac{C_1}{C_1 + C_2}\right) \cdot Q$ and $Q_2 = \left(\frac{C_2}{C_1 + C_2}\right) \cdot Q$
(5) If n identical capacitors each having capacitances C are connected in series with supply voltage V then Equivalent capacitance $C_{eq} = \frac{C}{n}$ and Potential difference across each capacitor $V = \frac{V}{n}$ .	(5) If n identical capacitors are connected in parallel Equivalent capacitance $C_{eq} = nC$ and Charge on each capacitor $Q' = \frac{Q}{n}$