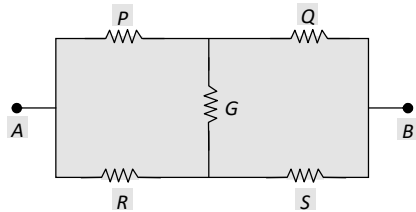


Some Standard Results for Equivalent Resistance.


(1) Equivalent resistance between points A and B in an unbalanced Wheatstone's bridge as shown in the diagram.

(i)



$$R_{AB} = \frac{PQ(R+S) + (P+Q)RS + G(P+Q)(R+S)}{G(P+Q+R+S) + (P+R)(Q+S)}$$

(ii)

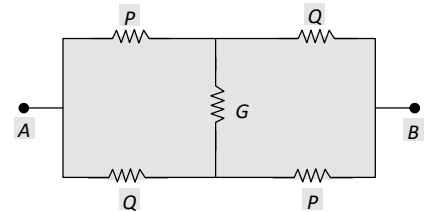

$$R_{AB} = \frac{2PQ + G(P+Q)}{2G + P + Q}$$

(2) A cube each side have resistance R then equivalent resistance in different situations

(i) Between E and C i.e. across the diagonal of the cube


$$R_{EC} = \frac{5}{6}R$$

(ii) Between A and B i.e. across one side of the cube

$$R_{AB} = \frac{7}{12}R$$


(iii) Between A and C i.e. across the diagonal of one face of the cube

$$R_{AC} = \frac{3}{4}R$$

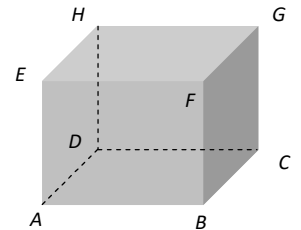


(3) The equivalent resistance of infinite network of resistances

(i)

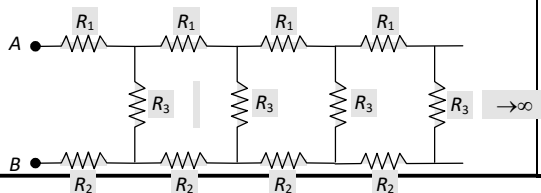

(ii)

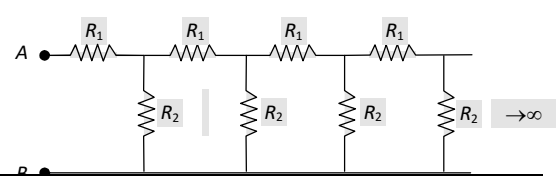

$$R_{AB} = \frac{1}{2}(R_1 + R_2) + \frac{1}{2} \left[(R_1 + R_2)^2 + 4R_3(R_1 + R_2) \right]^{1/2}$$

$$R_{AB} = \frac{1}{2} R_1 \left[1 + \sqrt{1 + 4 \left(\frac{R_2}{R_1} \right)} \right]$$

Concepts

If n identical resistances are first connected in series and then in parallel, the ratio of the equivalent

resistance is given by $\frac{R_p}{R_s} = \frac{n^2}{1}$.

If equivalent resistance of R1 and R2 in series and parallel be Rs and Rp respectively then

$$R_1 = \frac{1}{2} \left[R_s + \sqrt{R_s^2 - 4R_s R_p} \right] \text{ and } R_2 = \frac{1}{2} \left[R_s - \sqrt{R_s^2 - 4R_s R_p} \right].$$

If a wire of resistance R, cut in n equal parts and then these parts are collected to form a bundle then

equivalent resistance of combination will be $\frac{R}{n^2}$.