

Terms Related to ac Circuits.

(1) Resistance (R): The opposition offered by a conductor to the flow of current through it is defined as the resistance of that conductor. Reciprocal of resistance is known as conductance (G)



i.e.
$$G = \frac{1}{R}$$

(2) Impedance (Z): The opposition offered by the capacitor, inductor and conductor to the flow

of ac through it is defined as impedance. Its unit is ohm (Ω).

$$Z = \frac{V_0}{i_0} = \frac{V_{rms}}{i_{rms}}$$

(3) Reactance (X): The opposition offered by inductor or capacitor or both to the flow of ac through it is defined as reactance. It is of following two type –

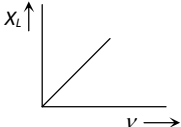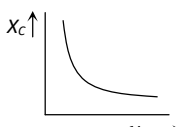Inductive reactance (XL)	Capacitive reactance (XC)
(i) Offered by inductive circuit	(i) Offered by capacitive circuit
(ii) $X_L = \omega L = 2\pi\nu L$	(ii) $X_C = \frac{1}{\omega C} = \frac{1}{2\pi\nu C}$
(iii) $\nu_{dc} = 0$ so for dc, $X_L = 0$	(iii) For dc $X_C = \infty$
(iv) X_L - ν Graph 	(iv) X_C - ν Graph 

Note: Resultant reactance of LC circuit is defined as $X = X_L \sim X_C$.

(4) Admittance (Y): Reciprocal of impedance is known as admittance $\left(Y = \frac{1}{Z}\right)$, its unit is mho.

(5) Susceptance (S): the reciprocal of reactance is defined as susceptance $\left(S = \frac{1}{X}\right)$, it is of two type

(i) Inductive susceptance $S_L = \frac{1}{X_L} = \frac{1}{2\pi\nu L}$ and (ii) Capacitive susceptance,

$$S_C = \frac{1}{X_C} = \omega C = 2\pi\nu C$$

.